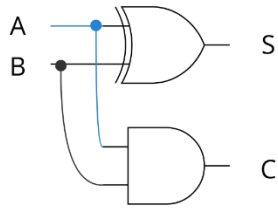


1.4.3 Adders Questions

2. This diagram shows the logic circuit for a **half** adder.




Complete the truth table for this half adder circuit.

A	B	S	C (Out)
0	0		
0	1		
1	0		
1	1		

[4]

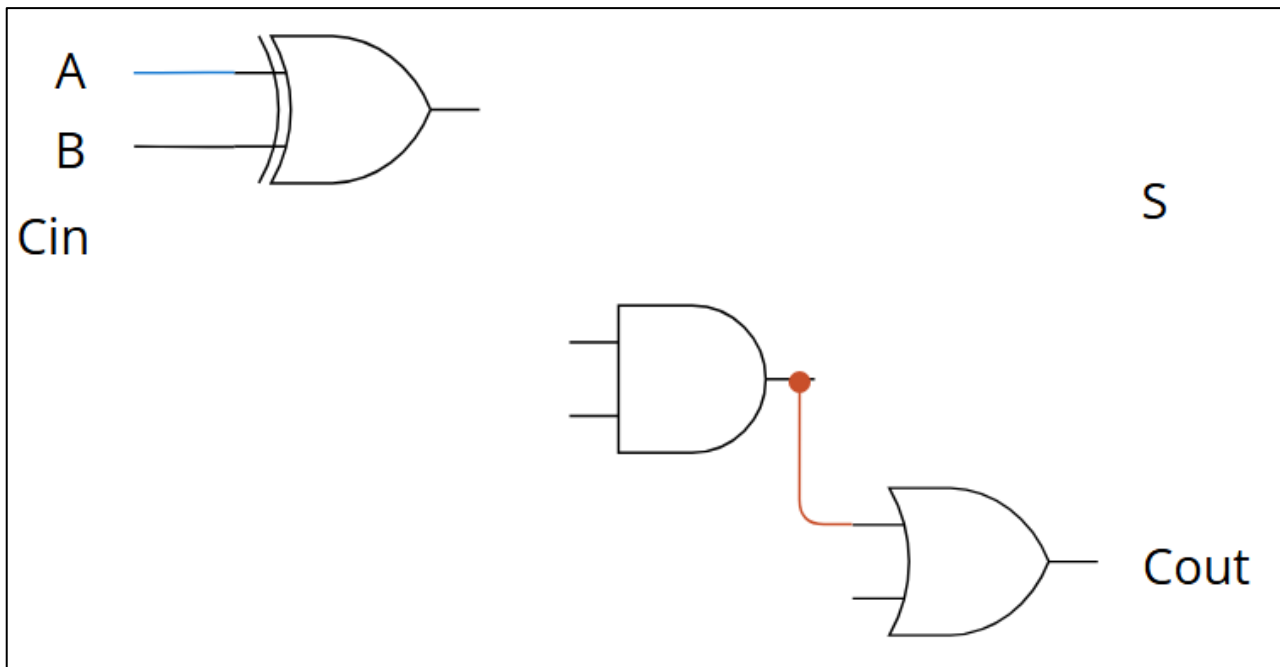2. The diagram below has missing components of a logic circuit for a full adder. Complete the missing components for a full adder circuit.



- i. Complete the table for a full adder circuit.

[5]

1.4.3 Adders Questions

ii. Complete the truth table for the full adder circuit


Inputs			Outputs	
A	B	Cin	Cout	S
0	0			
0	0			
0	1			
0	1			
1	0			
1	0			
1	1			
1	1			

[3]

END OF QUESTION PAPER

1.4.3 Adders Questions

Mark scheme

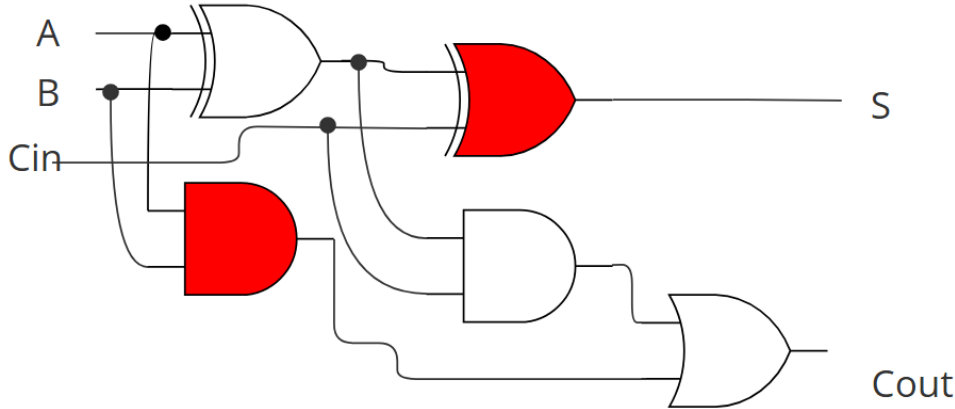Question			Answer/Indicative content	Marks	Guidance																				
1			1 mark for each correct row.	4																					
			<table><thead><tr><th>A</th><th>B</th><th>S</th><th>C</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr></tbody></table>	A	B	S	C	0	0	0	0	0	1	1	0	1	0	1	0	1	1	0	1		
A	B	S	C																						
0	0	0	0																						
0	1	1	0																						
1	0	1	0																						
1	1	0	1																						
2	I			3																					
			<ul style="list-style-type: none">1 mark for each missing component (in red)1 mark for correctly drawing both lines																						

1.4.3 Adders Questions

		ii	<table><tr><th colspan="3">Inputs</th><th colspan="2">Outputs</th></tr><tr><th>A</th><th>B</th><th>Cin</th><th>Cout</th><th>S</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr></table>	Inputs			Outputs		A	B	Cin	Cout	S	0	0	0	0	0	0	0	1	0	1	0	1	0	0	1	0	1	1	1	0	1	0	0	0	1	1	0	1	1	0	1	1	0	1	0	1	1	1	1	1	3	
Inputs			Outputs																																																				
A	B		Cin	Cout	S																																																		
0	0		0	0	0																																																		
0	0		1	0	1																																																		
0	1		0	0	1																																																		
0	1		1	1	0																																																		
1	0		0	0	1																																																		
1	0		1	1	0																																																		
1	1		0	1	0																																																		
1	1	1	1	1																																																			
		<ul style="list-style-type: none">• 1 mark for correctly filling out Cin column• 1 mark for correctly filling out Cout Column• 1 mark for correctly filling out S column																																																					
		Total	10																																																				