



## 1.4.3 D-Type Flip flops Questions

1. Fez has created a logic circuit. The expression he has created for the logic circuit is:


$$Q = (A \wedge \neg B) \vee (\neg A \wedge C) \vee (A \wedge B)$$

CIAB	00	01	11	10
0				
1				

What is the simplified expression?

\_\_\_\_\_ [4]

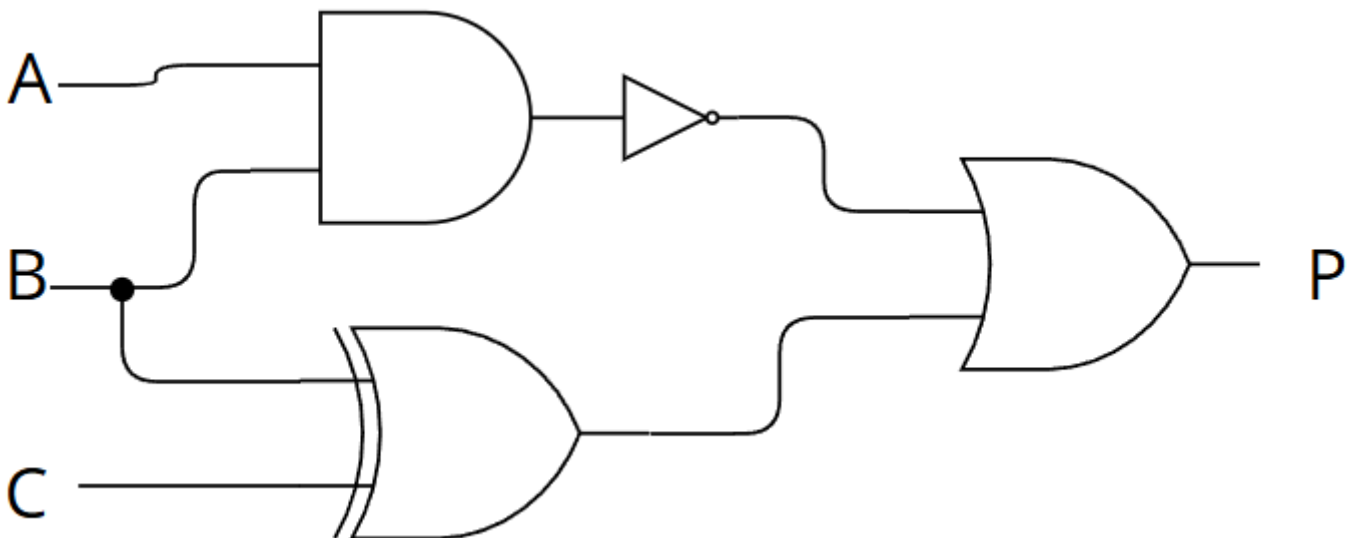2. A computer scientist has created the following logic circuit



Give the Boolean expression that represents the logic circuit shown above. Do not attempt to simplify the expression.

\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_ [2]



## 1.4.3 D-Type Flip flops Questions

3. (a) Complete the truth table for the logic circuit shown above.

A	B	C	P

[3]

(b) The following Karnaugh map represents another logic circuit.

CD\AB	00	01	11	10
00	1	1	1	1
01	0	0	1	1
11	0	0	0	0
10	1	1	0	0

Use this Karnaugh map to find the simplified expression for this circuit.  
You should highlight the map as appropriate and write the expression here.

---



---



---



---

[4]



### 1.4.3 D-Type Flip flops Questions

4. (a) Complete the Karnaugh map below for Boolean expression  $(A \wedge \neg B) \vee (D \wedge \neg C)$

CD\AB	00	01	11	10
00				
01				
11				
10				

[3]

- (b) Use the Karnaugh map to see if a simplified expression can be found.

[2]

END OF QUESTION PAPER



## 1.4.3 D-Type Flip flops Questions

### Mark scheme

Question			Answer/Indicative content	Marks	Guidance																																								
1			<table><tr><td>C\AB</td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td></td><td></td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr></table> <p>1 mark per bullet up to a maximum of 4 marks:</p> <ul style="list-style-type: none"><li>1 mark for filling in the table correctly</li><li>1 mark for the group shown in red</li><li>1 mark for the group shown in blue</li><li>1 mark for the simplified expression <b>AVC</b></li></ul>	C\AB	00	01	11	10	0			1	1	1	1	1	1	1	4																										
C\AB	00	01	11	10																																									
0			1	1																																									
1	1	1	1	1																																									
2			<ul style="list-style-type: none"><li><math>\neg(A \wedge B)</math></li><li><math>v (B \vee C)</math></li></ul>	2																																									
3	a		<table><tr><td>A</td><td>B</td><td>C</td><td>P</td><td>Marking Guidance</td></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td rowspan="2">1 mark</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td><td rowspan="2">1 mark</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td rowspan="4">1 mark</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	P	Marking Guidance	0	0	0	1	1 mark	0	0	1	1	0	1	0	1	1 mark	0	1	1	1	1	0	0	1	1 mark	1	0	1	1	1	1	0	1	1	1	1	0	3	
A	B	C	P	Marking Guidance																																									
0	0	0	1	1 mark																																									
0	0	1	1																																										
0	1	0	1	1 mark																																									
0	1	1	1																																										
1	0	0	1	1 mark																																									
1	0	1	1																																										
1	1	0	1																																										
1	1	1	0																																										
3	b		<table><tr><td>CD\AB</td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>1</td><td>1</td><td>1</td><td>1</td></tr><tr><td>01</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>11</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>10</td><td>1</td><td>1</td><td>0</td><td>0</td></tr></table> <ul style="list-style-type: none"><li>Correct highlighting on K-map as shown above</li><li><math>(A \wedge \neg D)</math></li><li><math>(A \wedge \neg C)</math></li><li>Expressions joined with <math>v</math> // OR</li></ul>	CD\AB	00	01	11	10	00	1	1	1	1	01	0	0	1	1	11	0	0	0	0	10	1	1	0	0	4																
CD\AB	00	01	11	10																																									
00	1	1	1	1																																									
01	0	0	1	1																																									
11	0	0	0	0																																									
10	1	1	0	0																																									

## 1.4.3 D-Type Flip flops Questions

4	a	<ul style="list-style-type: none"> <li>Left column filled as <math>(A \wedge \neg B)</math></li> <li>2<sup>nd</sup> row filled as <math>(D \wedge \neg C)</math></li> <li>Other cells filled as zero or left blank</li> </ul> <table border="1"> <thead> <tr> <th>CD\AB</th><th>00</th><th>01</th><th>11</th><th>10</th></tr> </thead> <tbody> <tr> <td>00</td><td>1</td><td></td><td></td><td></td></tr> <tr> <td>01</td><td>1</td><td></td><td></td><td></td></tr> <tr> <td>11</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr> <td>10</td><td>1</td><td></td><td></td><td></td></tr> </tbody> </table>	CD\AB	00	01	11	10	00	1				01	1				11	1	1	1	1	10	1				3	
CD\AB	00	01	11	10																									
00	1																												
01	1																												
11	1	1	1	1																									
10	1																												
4	b	<p>1 mark for:</p> <ul style="list-style-type: none"> <li>Karnaugh map used to highlight 1s on the map</li> <li>Expression cannot be simplified.</li> </ul> <table border="1"> <thead> <tr> <th>CD\AB</th><th>00</th><th>01</th><th>11</th><th>10</th></tr> </thead> <tbody> <tr> <td>00</td><td>1</td><td></td><td></td><td></td></tr> <tr> <td>01</td><td>1</td><td></td><td></td><td></td></tr> <tr> <td>11</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr> <td>10</td><td>1</td><td></td><td></td><td></td></tr> </tbody> </table>	CD\AB	00	01	11	10	00	1				01	1				11	1	1	1	1	10	1				2	
CD\AB	00	01	11	10																									
00	1																												
01	1																												
11	1	1	1	1																									
10	1																												
		<b>Total</b>	<b>10</b>																										