



1.4.3 Karnaugh Maps Questions

1. Fez has created a logic circuit. The expression he has created for the logic circuit is:


$$Q = (A \wedge \neg B) \vee (\neg A \wedge C) \vee (A \wedge B)$$

CIAB	00	01	11	10
0				
1				

What is the simplified expression?

_____ [4]

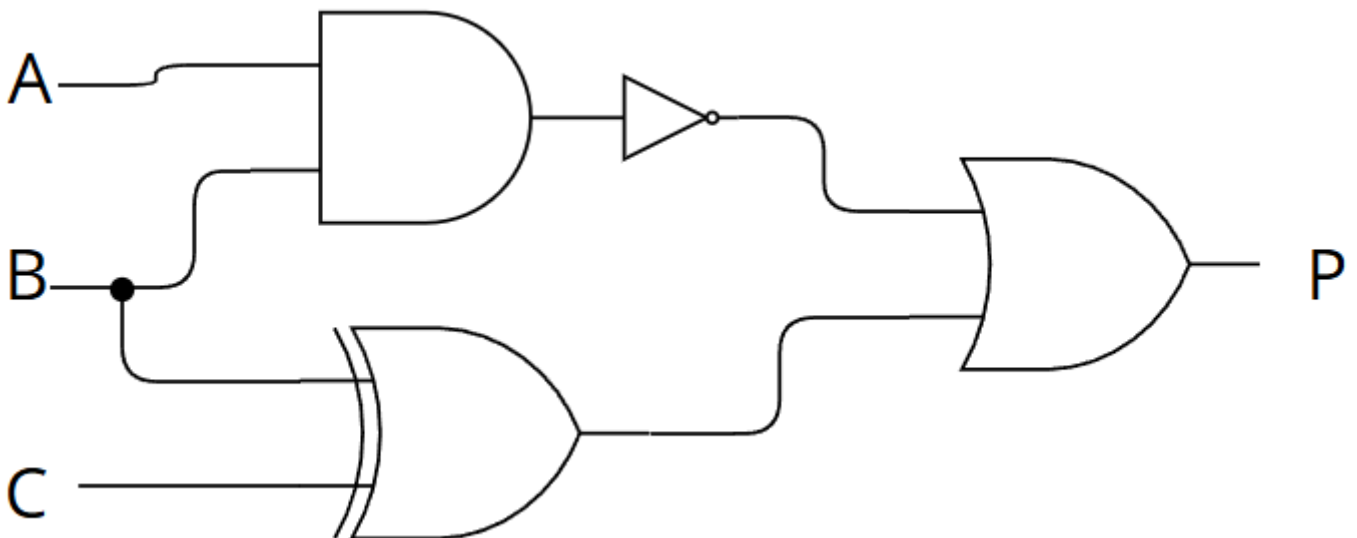2. A computer scientist has created the following logic circuit



Give the Boolean expression that represents the logic circuit shown above. Do not attempt to simplify the expression.

 _____ [2]



1.4.3 Karnaugh Maps Questions

3. (a) Complete the truth table for the logic circuit shown above.

A	B	C	P

[3]

(b) The following Karnaugh map represents another logic circuit.

CD\AB	00	01	11	10
00	1	1	1	1
01	0	0	1	1
11	0	0	0	0
10	1	1	0	0

Use this Karnaugh map to find the simplified expression for this circuit.
You should highlight the map as appropriate and write the expression here.

[4]



1.4.3 Karnaugh Maps Questions

4. (a) Complete the Karnaugh map below for Boolean expression $(A \wedge \neg B) \vee (D \wedge \neg C)$

CD\AB	00	01	11	10
00				
01				
11				
10				

[3]

- (b) Use the Karnaugh map to see if a simplified expression can be found.

[2]

END OF QUESTION PAPER



Mark scheme

Question			Answer/Indicative content	Marks	Guidance																																								
1			<table><tr><td>C\AB</td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>0</td><td></td><td></td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr></table> <p>1 mark per bullet up to a maximum of 4 marks:</p> <ul style="list-style-type: none">1 mark for filling in the table correctly1 mark for the group shown in red1 mark for the group shown in blue1 mark for the simplified expression AVC	C\AB	00	01	11	10	0			1	1	1	1	1	1	1	4																										
C\AB	00	01	11	10																																									
0			1	1																																									
1	1	1	1	1																																									
2			<ul style="list-style-type: none">$\neg(A \wedge B)$$v (B \vee C)$	2																																									
3	a		<table><tr><td>A</td><td>B</td><td>C</td><td>P</td><td>Marking Guidance</td></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td rowspan="2">1 mark</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td><td rowspan="2">1 mark</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td rowspan="4">1 mark</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	P	Marking Guidance	0	0	0	1	1 mark	0	0	1	1	0	1	0	1	1 mark	0	1	1	1	1	0	0	1	1 mark	1	0	1	1	1	1	0	1	1	1	1	0	3	
A	B	C	P	Marking Guidance																																									
0	0	0	1	1 mark																																									
0	0	1	1																																										
0	1	0	1	1 mark																																									
0	1	1	1																																										
1	0	0	1	1 mark																																									
1	0	1	1																																										
1	1	0	1																																										
1	1	1	0																																										
3	b		<table><tr><td>CD\AB</td><td>00</td><td>01</td><td>11</td><td>10</td></tr><tr><td>00</td><td>1</td><td>1</td><td>1</td><td>1</td></tr><tr><td>01</td><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>11</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>10</td><td>1</td><td>1</td><td>0</td><td>0</td></tr></table> <ul style="list-style-type: none">Correct highlighting on K-map as shown above$(A \wedge \neg D)$$(A \wedge \neg C)$Expressions joined with v // OR	CD\AB	00	01	11	10	00	1	1	1	1	01	0	0	1	1	11	0	0	0	0	10	1	1	0	0	4																
CD\AB	00	01	11	10																																									
00	1	1	1	1																																									
01	0	0	1	1																																									
11	0	0	0	0																																									
10	1	1	0	0																																									

1.4.3 Karnaugh Maps Questions

4	a	<ul style="list-style-type: none"> Left column filled as $(A \wedge \neg B)$ 2nd row filled as $(D \wedge \neg C)$ Other cells filled as zero or left blank <table border="1"> <thead> <tr> <th>CD\AB</th><th>00</th><th>01</th><th>11</th><th>10</th></tr> </thead> <tbody> <tr> <th>00</th><td>1</td><td></td><td></td><td></td></tr> <tr> <th>01</th><td>1</td><td></td><td></td><td></td></tr> <tr> <th>11</th><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr> <th>10</th><td>1</td><td></td><td></td><td></td></tr> </tbody> </table>	CD\AB	00	01	11	10	00	1				01	1				11	1	1	1	1	10	1				3	
CD\AB	00	01	11	10																									
00	1																												
01	1																												
11	1	1	1	1																									
10	1																												
4	b	<p>1 mark for:</p> <ul style="list-style-type: none"> Karnaugh map used to highlight 1s on the map Expression cannot be simplified. <table border="1"> <thead> <tr> <th>CD\AB</th><th>00</th><th>01</th><th>11</th><th>10</th></tr> </thead> <tbody> <tr> <th>00</th><td>1</td><td></td><td></td><td></td></tr> <tr> <th>01</th><td>1</td><td></td><td></td><td></td></tr> <tr> <th>11</th><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr> <th>10</th><td>1</td><td></td><td></td><td></td></tr> </tbody> </table>	CD\AB	00	01	11	10	00	1				01	1				11	1	1	1	1	10	1				2	
CD\AB	00	01	11	10																									
00	1																												
01	1																												
11	1	1	1	1																									
10	1																												
		Total	10																										